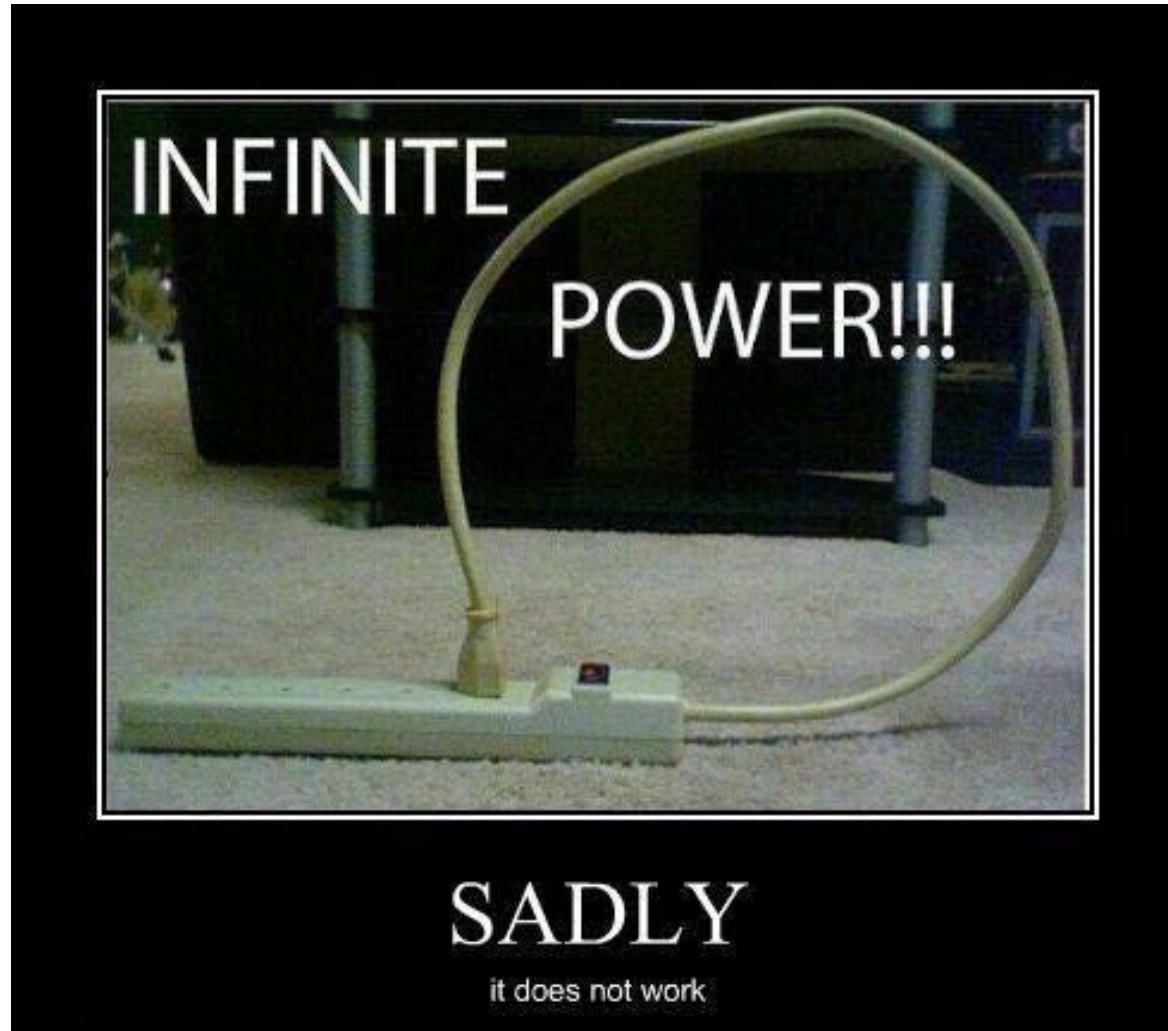


# Diagramming Circuits



# The Parts of an Electric Circuit...

For current electricity to occur, we must have a CIRCUIT - a PATHWAY for electricity to FLOW.

## 1. Energy Source:

- Place where the CURRENT comes from
- BATTERY, GENERATOR, TURBINE, WALL OUTLETS, etc.

## 2. Electrical Load:

- Anything that converts ELECTRICAL ENERGY into another form of ENERGY. → RESISTORS, LIGHT BULBS


## 3. Control Device:

- - SWITCHES, THERMOSTATS, etc.

## 4. Connectors:

- WIRES


### Four Parts of the Circuit

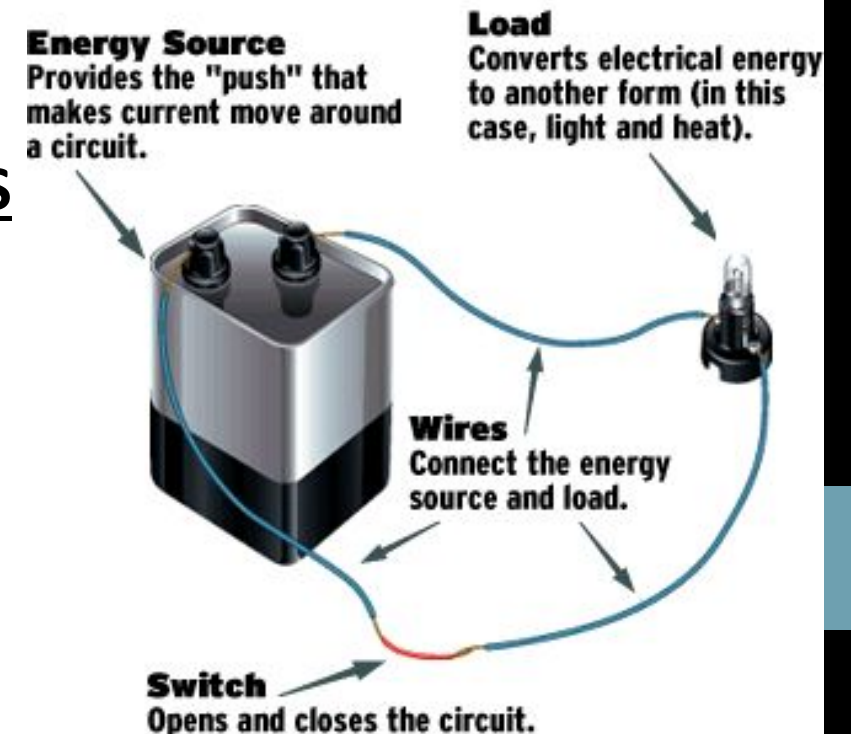

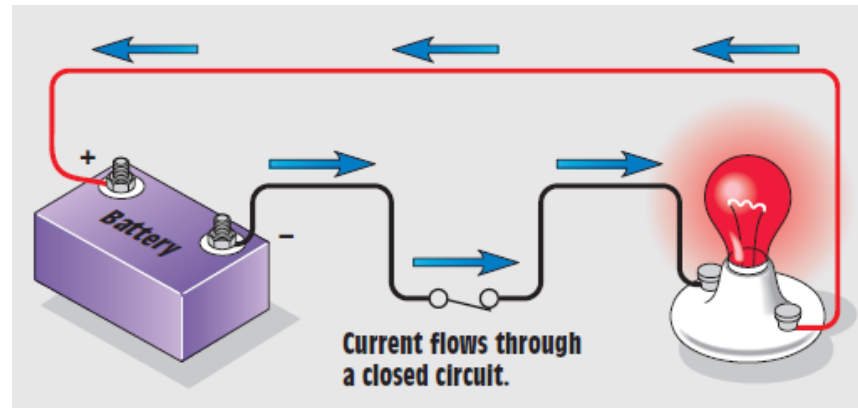
# Circuits...

A circuit usually forms a “**LOOP**” from the **ENERGY SOURCE** through **WIRES** and back to the **POWER SOURCE** or to the **GROUND**. A circuit can be:

- **CLOSED** - A circuit that is **OPERATING**, the **PATHWAY** is **COMPLETE**.



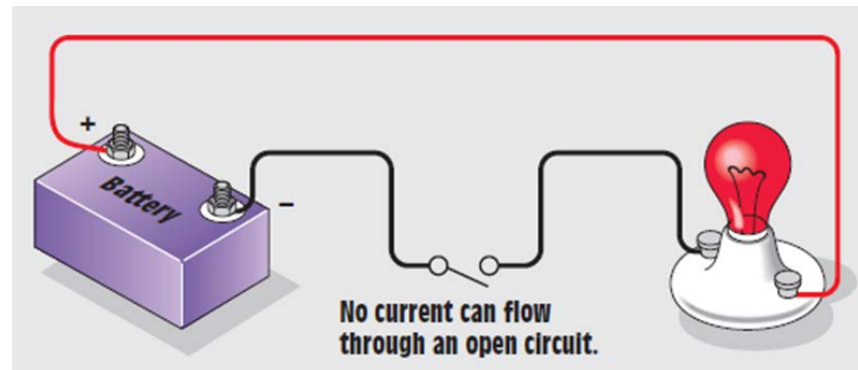
- **OPEN** - A circuit that is **NOT OPERATING**, the **PATHWAY** is **NOT COMPLETE**.




# Types of Circuits...

There are two main types of circuits:

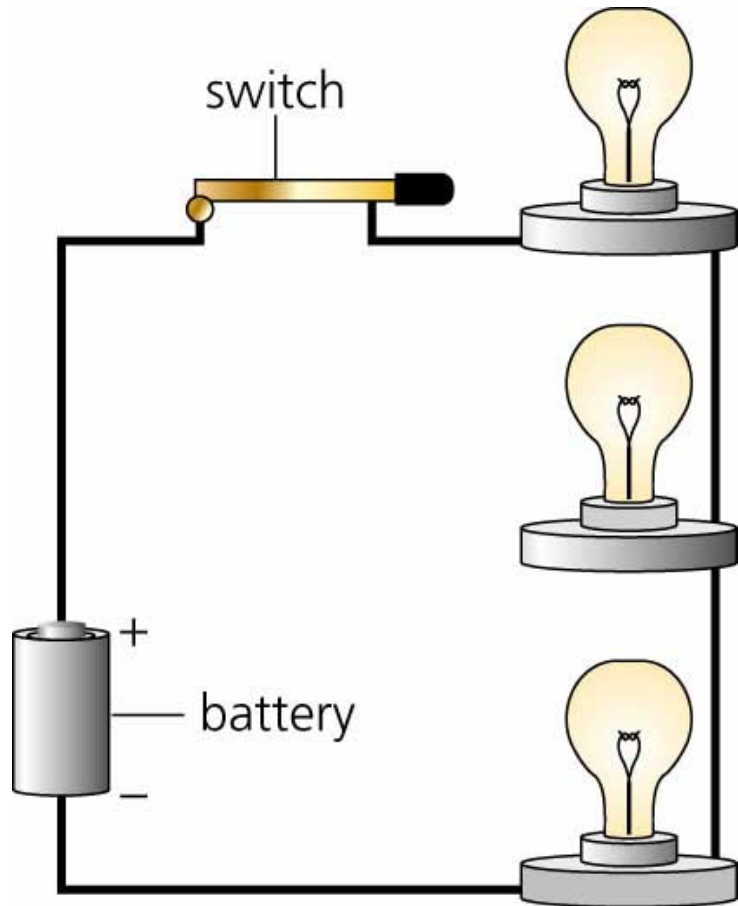**1. SERIES** – Only **ONE PATHWAY** for electrons to flow.





Academy Artworks

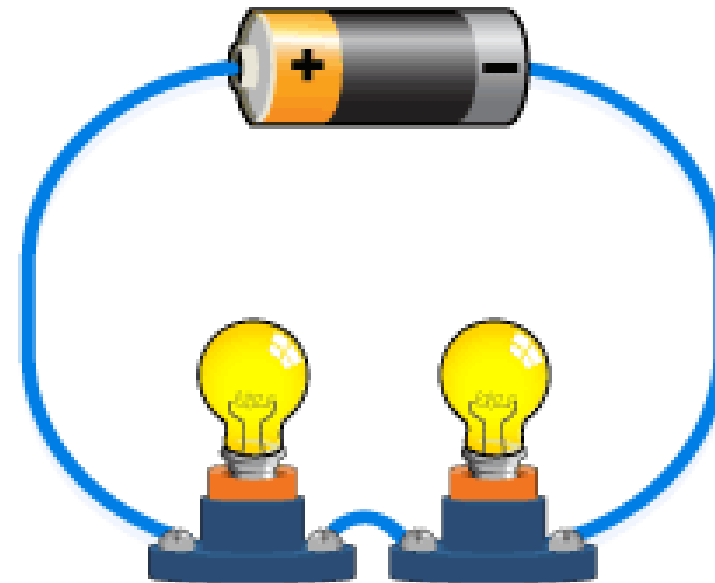



# Types of Circuits...

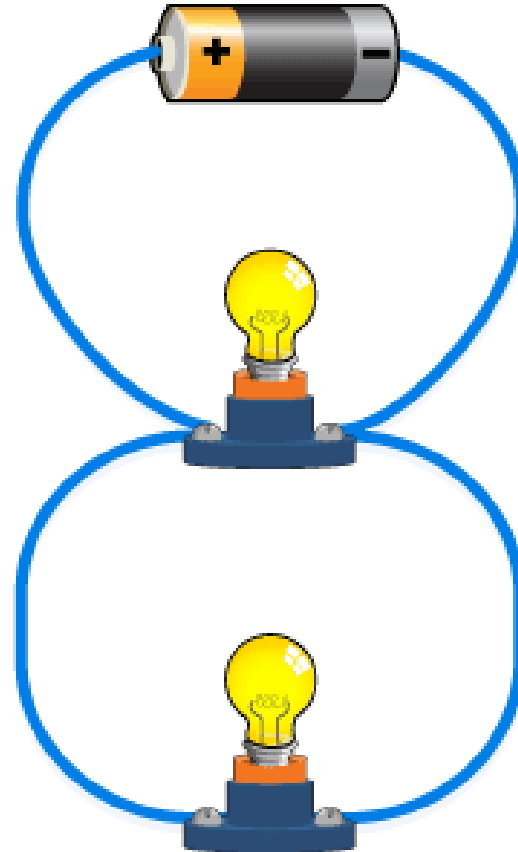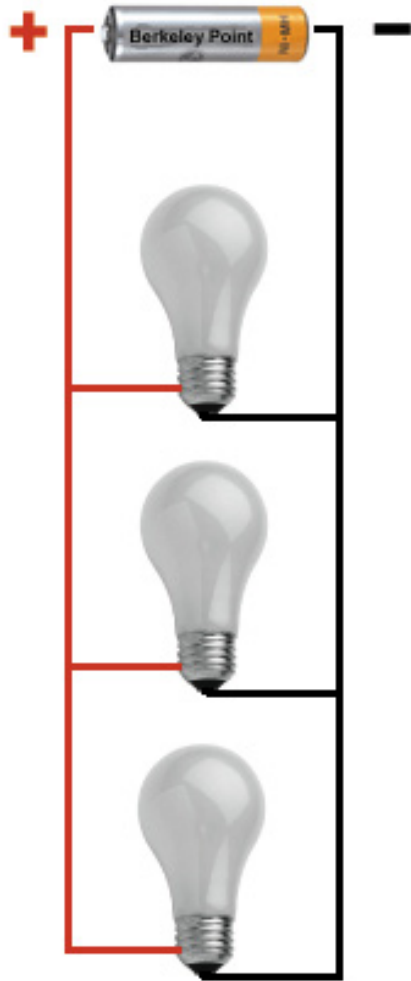2. PARALLEL – TWO or MORE PATHWAYS for electrons to flow.


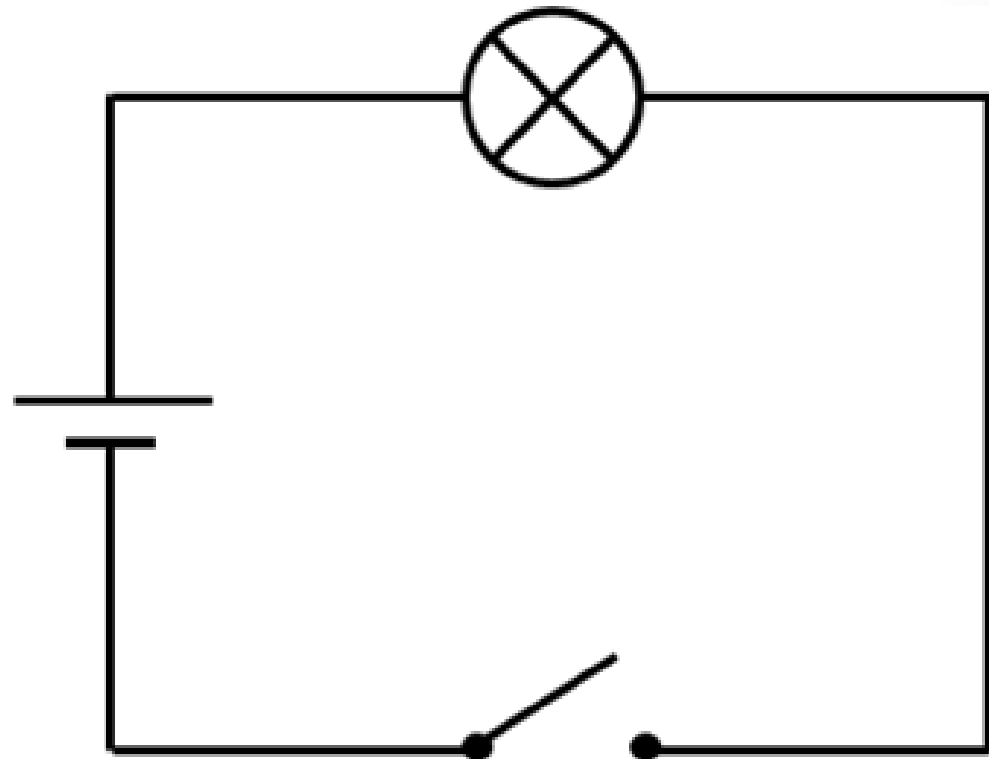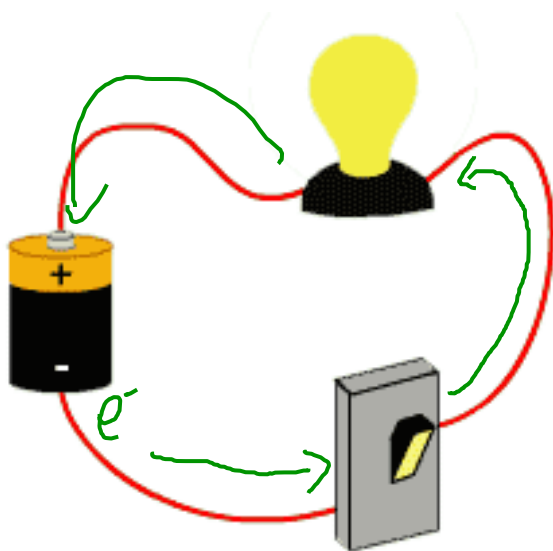
# Rules for Drawing Circuit Diagrams...

- Electrons **FLOW** from **NEGATIVE TO POSITIVE**.
- The **SWITCH** should be the **FIRST THING** that the electrons go through.
- **AMMETERS** (current) – are wired in **SERIES**.
- **VOLTMETERS** (pot. difference) – are wired in **PARALLEL**.
- **VOLTAGE RISE** = Voltage of the **CELL**,
- **VOLTAGE DROP** = Voltage across a **LOAD**




# Circuit Schematic Diagrams...

Scientists and electricians have developed a standard method of drawing circuits using what are called **SCHEMATIC SYMBOLS**. The following are the major symbols you will encounter:





Switch

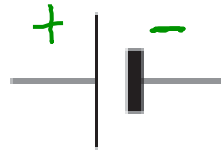

Cell



Battery

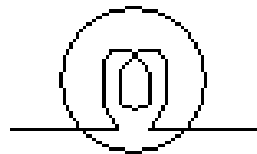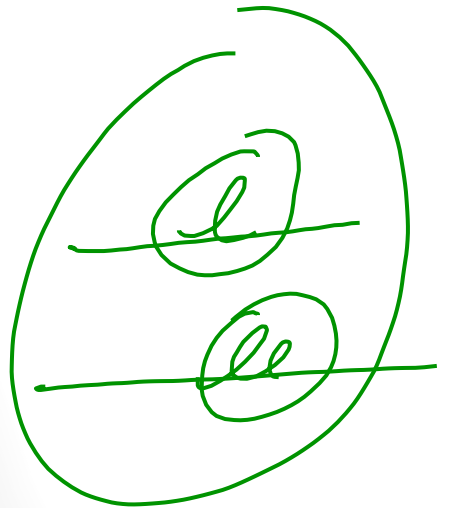

Lamp



Voltmeter



Ammeter

wire



Resistor



Motor


# Circuits in Series...

- Electrons have only **ONE PATH** to flow (like a **RACE TRACK**).
- If there is a **BREAK** in the circuit, electrons will **NOT FLOW**.

**Build and Draw the following circuit:**

1 switch, 2 bulbs in series, 1 cell.

4 wires

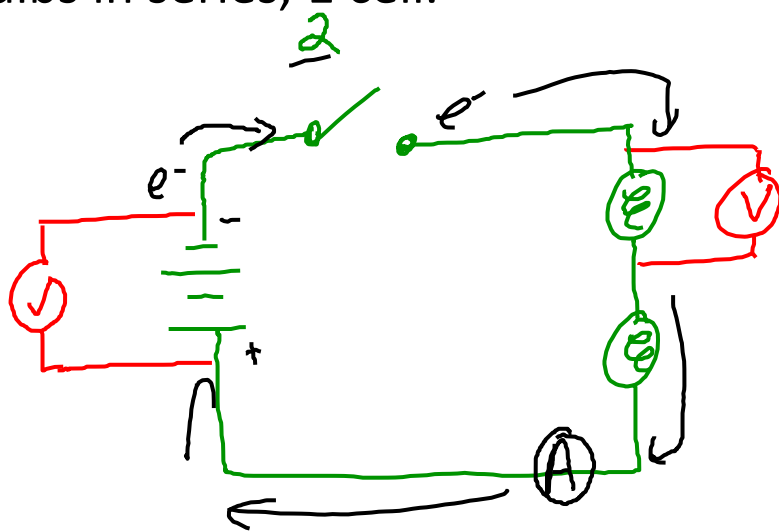

Now use a multimeter to measure the **voltage rise**, **voltage drop**, and the **current** of the circuit. Then draw the placement of the multimeter above.

$$\begin{aligned}
 V_{\text{Rise}} &= 2.5 \text{ V} \\
 V_{\text{Drop 1}} &= 1.1 \text{ V} \\
 I &= 0.2 \text{ A}
 \end{aligned}
 \quad + \quad V_{\text{Drop 2}} = 1.34 \text{ V} \quad \leftarrow \quad \text{2.44 V}$$




# Circuits in Parallel...

- Electrons have MORE THAN ONE path to flow (like CITY STREETS).
- If there is a BREAK in the circuit, electrons WILL CONTINUE to FLOW.

**Build and Draw the following circuit:**

1 switch, 2 bulbs in parallel,  $\frac{1}{2}$  cell.

5 wires

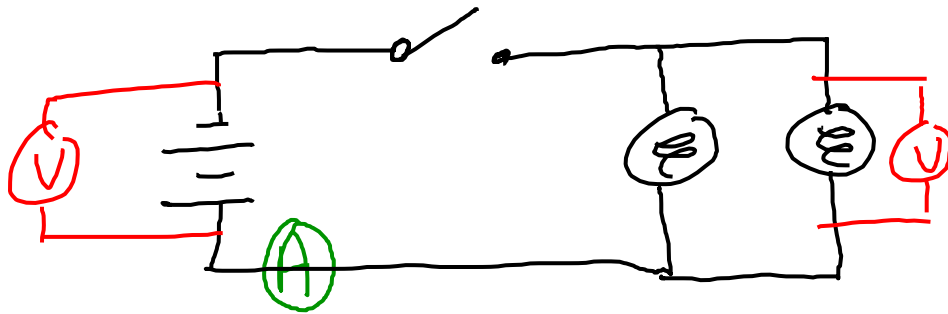

Now use a multimeter to measure the **voltage rise**, **voltage drop**, and the **current** of the circuit. Then draw the placement of the multimeter above.

$$\begin{aligned} V_{\text{Rise}} &= 2.4 \text{ V} \\ V_{\text{Drop}_1} &= 2.11 \text{ V} \\ I &= 0.59 \text{ A} \end{aligned}$$




$$V_{\text{Drop}_2} = 1.95 \text{ V}$$

# Cells in Series & Parallel...

We can wire our CELLS in different ways.
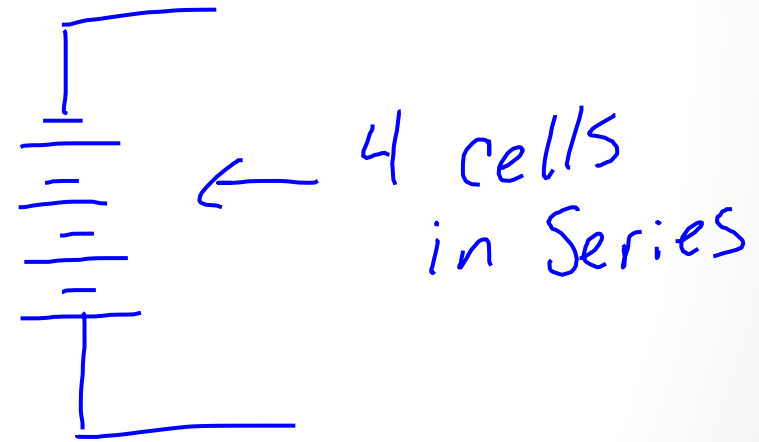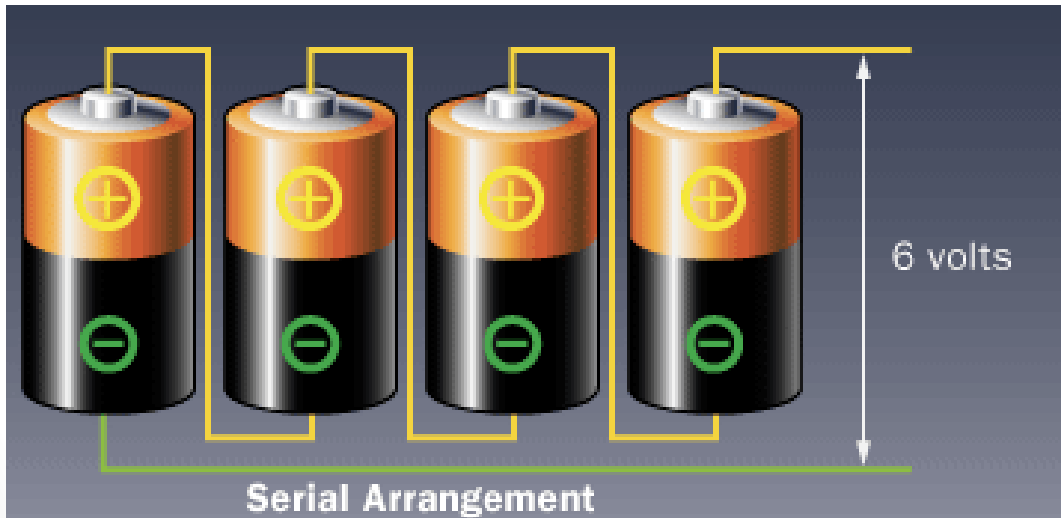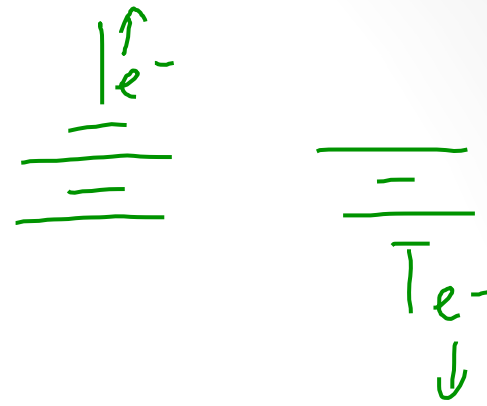
## Cells in Series:

- Cells wired in series gives an INCREASED VOLTAGE.
- BATTERIES are made of different cells wired together in series.



# Cells in Series & Parallel...

## Cells in Parallel:

- Cells in **PARALLEL DO NOT** increase voltage.
- Cells in parallel **LAST MUCH LONGER** because **VOLTAGE** is **DIVIDED** between the **TWO** (or more) cells.

